
 


Ashaki Gumbs
Sequence Detector

 - A. Files for FPGA Implementation can be found here: [Quartus FPGA Implementation](#)
 - a. Files for Xilinx Synthesis can be found [here](#) and in this Microsoft Word Document:
- B. Finite State Machine



C. Wiring Schematic



D. Write System Verilog description of transmitter circuit

```
assign serOut = (counter != 0)? serIn: 1'bz;
```

Figure 1: Transmitter

E. Write System Verilog description of sequence detector.

```
always @ (posedge clk or posedge rst)begin
    if (rst) current_state <= S0;
    else
        current_state <= next_state;
    $display("Current state is: %d", current_state);
End

always@(current_state, serIn, serOutValid, counter)begin
    case(current_state)
        S0:if (serIn==0) next_state <= S1; else next_state <= S0;
        S1:if (serIn==1) next_state <= S2; else next_state <= S1;
        S2:if (serIn==1) next_state <= S3; else next_state <= S1;
        S3:if (serIn==1) next_state <= S4; else next_state <= S1;
        S4:if (serIn==1) next_state <= S5; else next_state <= S1;
        S5:if (serIn==0) next_state <= S6; else next_state <= S5;
        S6:if (counter == 1023) next_state <= S0; else next_state <= S6; // sequence detected
    endcase
end

assign serOutValid = (current_state == S6)? 1: 0; //if in S6, start counter
```

F. Write SystemVerilog Description of Counter

```
logic [10:0] counter; //1024 clock cycles
always@(posedge clk or posedge rst) begin
    if(rst) begin
        counter <= 0;
    end else if (serOutValid==1 && clk == 1)begin
        counter <= counter + 1'b1;
    end
end
end
```

G. Write the SystemVerilog Description of the testbench: ***Continued on next page...***

Ashaki Gumbs
Sequence Detector

```
module Top_Test();
reg In;
reg clk;
reg rst;
wire Out;
int p;
logic[10:0] i;

Top uut(.serIn(In), .clk(clk), .rst(rst), .serOut(Out));

//Detect Sequence//
initial begin
clk = 0;
rst = 0;
In = 1'bz;
#10
rst = 1;
#10
rst = 0;
#10
In = 1'b0;
#10
In = 1'b1;
#10
In = 1'b1;
#10
In = 1'b1;
#10
In = 1'b1;
#10
In = 1'b0;
#10
In = 1'b1;

//Sequence Detected
#10
In = 1'b0;
#10
for(i = 0; i <= 1024; i = i +1)begin
#10
In = $urandom_range(1,0);

end
end


always # 5 clk = ~clk;
endmodule
```

Ashaki Gumbs
Sequence Detector

Simulation when sequence detected



Transmit when sequence detected

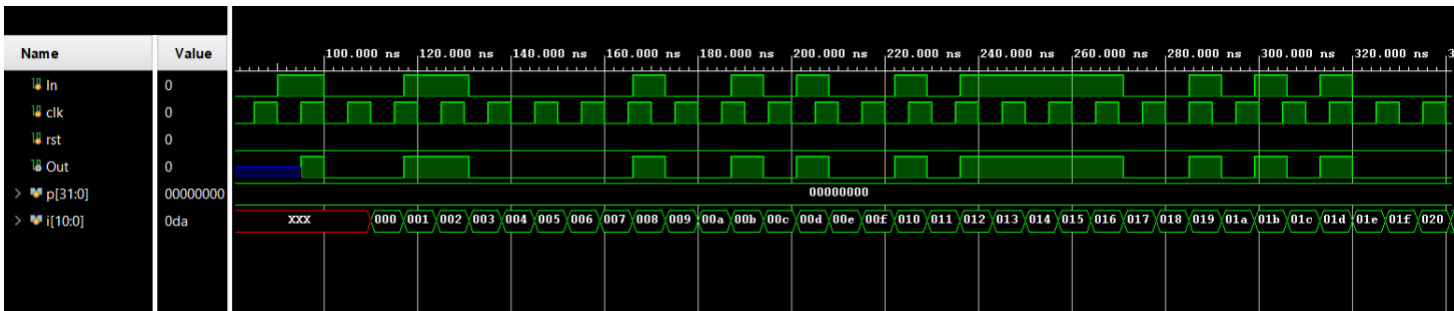

1024-clock cycles once sequence is detected...

